

EECS112L Organization of Digital Computers Lab

Final Project Pipeline ARM

Group name: Three Musketeers

Group ID: 118

Student name:
Raymond Wang
Jared Lim
Heyang Chen

Student ID:
17769107
31633414
55554499

EECS Department
Henry Samueli School of Engineering
University of California, Irvine


March, 24, 2017

1 Description of this Lab


In this lab, We implemented a five stage pipeline processor according to the single cycle ARM processor we designed in last lab.

2 Block Diagram

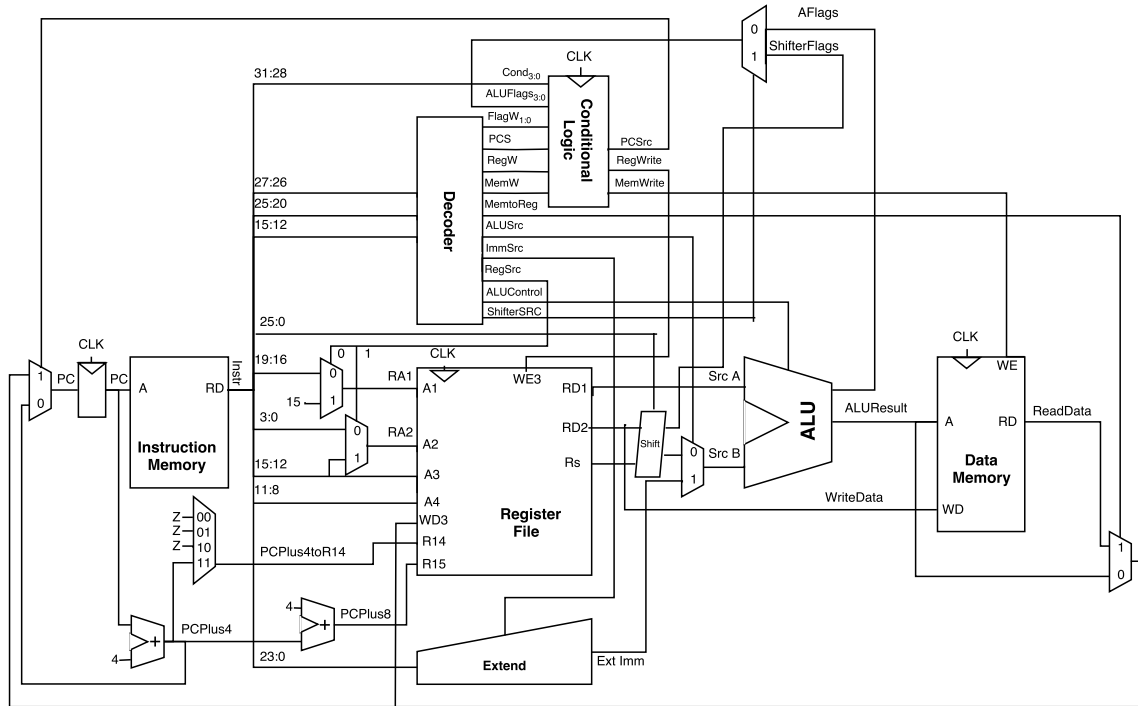This is the block diagram of the single cycle processor from last time.



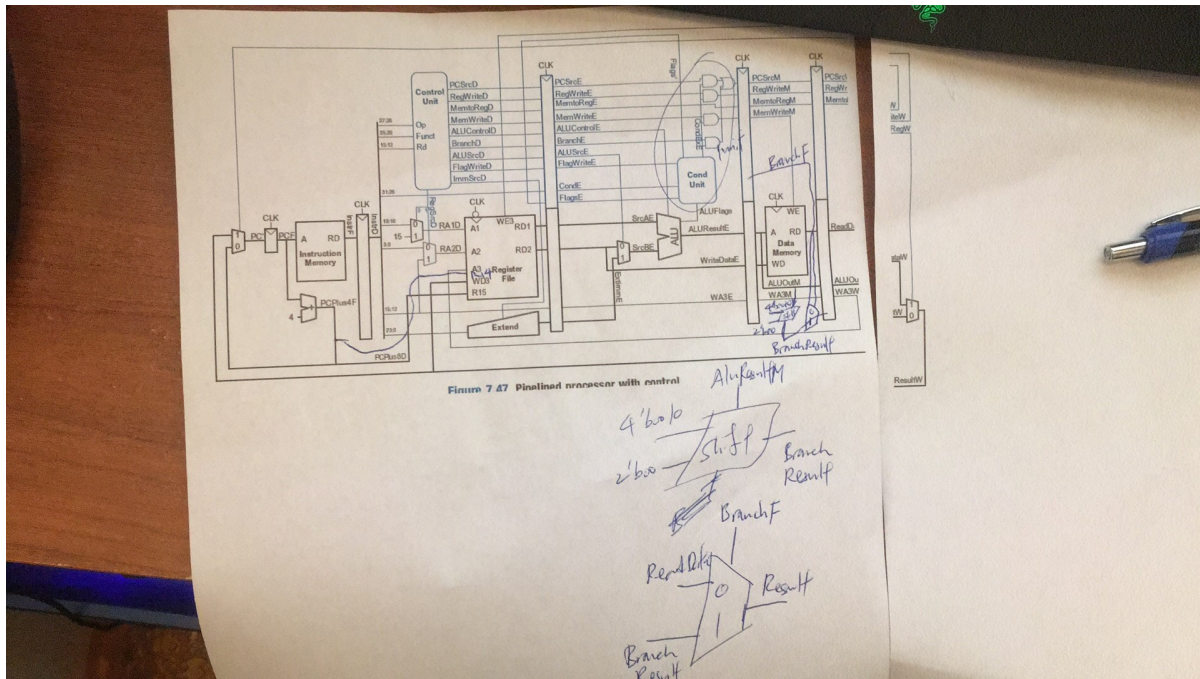This is the block diagram of pipeline processor with control.



3 Design Architecture

For the design of five stage pipeline processor, it is separated in three steps as indicated in project description.

First of all, we have designed four pipeline registers, which separate a single cycle processor into five stages, Fetch, Decode, Execute, Memory, and Writeback. These pipeline registers takes not only logics coming out from modules such as regfile, ALU but also takes control signals. Also in this step, we have the conditional logic separated from its formal place control unit but put it individually in execute stage as conditional unit.

In the second stage, we design a hazard unit, which takes signal regwrite at both memory stage and writeback stage, and also 4 matching signals. Then it output ForwardAE and ForwardBE, which are signals to use in two 4 way multiplexer to decide whether the result can be directly forward back to use as SrcA or SrcB.

At last, we edited hazard unit by adding one more matching signal input, and memtoreg signal at execute stage into it, while also having it output StallF, StallD and FlushE. When these signals are received in pipeline register, the pipeline register will stall the current situation and add NOP into it. When stall ends, the pipeline register will work again.

4 Simulation Waveform